

Quartz Crystal Oscillator Implementation with PolarPro and Eclipse II



••••• QuickLogic® Application Note 95

Introduction

This application note provides relevant information for designers who want to compare the performance of quartz crystal oscillators to self-contained oscillators when implementing their designs on PolarPro and Eclipse II devices. All data presented has been verified using a QuickLogic internal test board. A PCB layout is included as a crucial part in correct oscillator design.

The quartz crystal oscillator implementation is selected with the intent to reduce manufacturing costs and to save board space.

Quartz Crystal Oscillator Circuit

The suggested configuration to support the quartz crystals is illustrated in **Figure 1**. This method is recommended for frequencies less than 30 MHz.

Table 1 shows the optimal value of components for various frequencies. Note that R_d is only dependant variable listed. All measurements are taken at $V_{cc} = \pm 3.3V$.

Figure 1: Crystal Oscillator Schematic

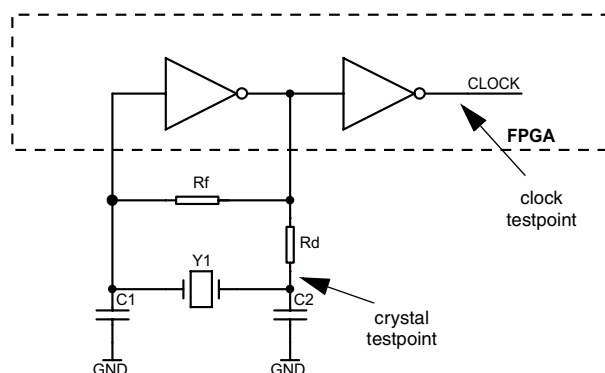


Table 1: Quartz Crystal Oscillator Frequencies—Fundamental Mode

Frequency	Device	Crystal	C1,C2	Rf	Rd
12 MHz	QL8150	Y1	15 pF	1 M	1.8 K
13 MHz	QL1P100-144	Y1	15 pF	1 M	1.8 K
14 MHz	QL8150	Y1	15 pF	1 M	1 K
16 MHz	QL1P100-144	Y1	15 pF	1 M	1 K
18 MHz	QL1P100-144	Y1	15 pF	1 M	1 K
25 MHz	QL8150	Y1	15 pF	1 M	560
27 MHz	QL1P100-144	Y1	15 pF	1 M	560

Test Results

Crystal Components

QuickLogic testing was done on quartz crystals from different manufacturers. For results shown in this application note the ECS Inc. HC-49USX quartz crystals were used. Crystals with a frequency range between 4 MHz to 30 MHz (in fundamental mode) were selected.

Waveform Results

Figure 2 shows 16 MHz and 25 MHz waveforms measured with a 1 GHz Tektronix TDS580D oscilloscope. The signal is measured near C2, see **Figure 1**.

Figure 2: Crystal Waveforms


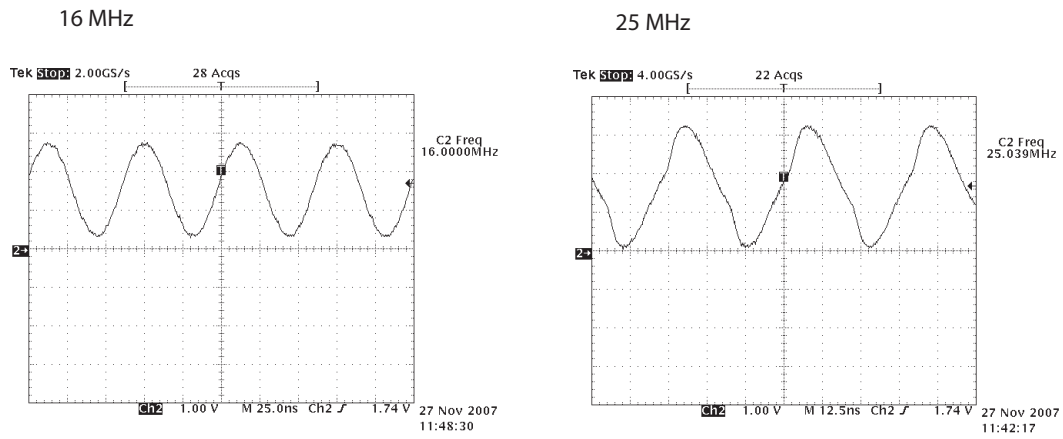



Figure 3 shows the same 16 MHz and 25 MHz clock signals on the output by the oscillator circuit. The signals are stable with low jitter and good swing. The overshooting and undershooting peaks are the result of imperfect line termination.

Figure 3: .Device Output Signals

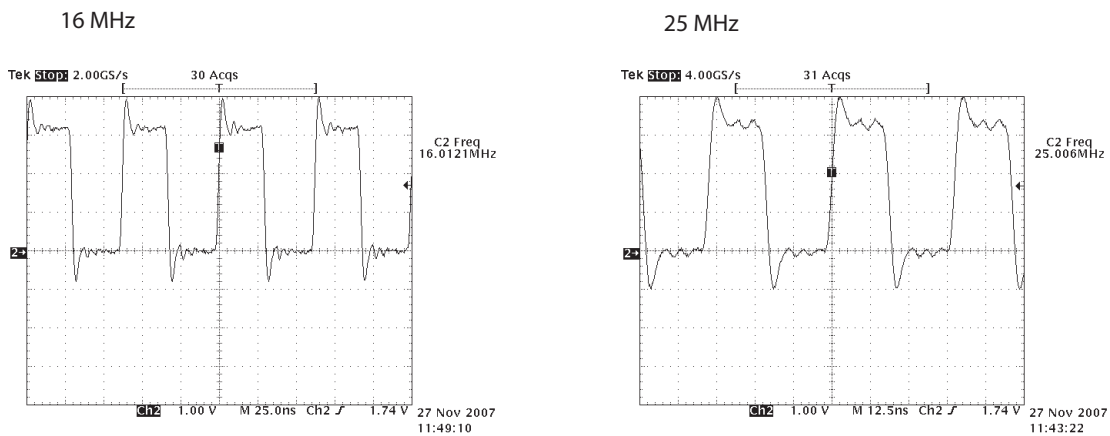

Crystal PCB Layout Recommendations

Figure 4 shows the reference PCB layout.

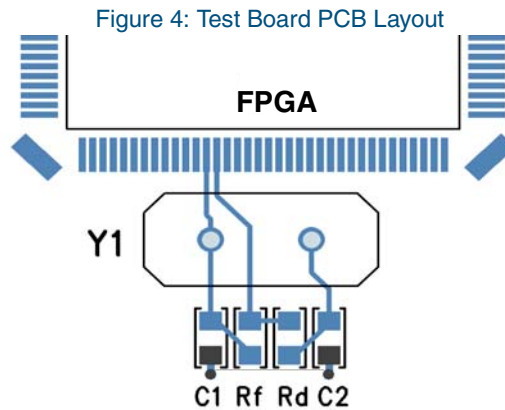

The following tips help with PCB layout design. Careful routing and placement of components are required for a successful layout.

- First place the crystal component as close as possible to the FPGA on the same side of the PCB.
- Second place the coupling capacitors and termination resistors as close as possible to the crystal, see **Figure 4**.
- Reduce noise by placing a ground plane under the crystal circuit. Adding a ground ring around the oscillator components is preferable.
- Provide good power decoupling as close as possible to the FPGA.
- Do not cross any clock traces on nearby layers.
- Avoid routing high speed, high noise and high power signals near the crystal oscillator circuit.

Additional Design Support

Getting Information About Quartz Crystal Selection

This application note assumes a basic understanding of the behavior and operation of quartz crystals and their design considerations. When using quartz crystal oscillators in an application it is important to be aware of the ASIC and crystal characteristics, and the circuit design requirements when selecting a crystal. For example, details such as input and output resistances, the mode of operation, typical crystal aging and so forth will have different effects in the application.

NOTE: For more information about the characteristics affected for each area of consideration see the [Abracon Quartz Crystals Application Note](http://www.abracon.com/Support/quartz_crystals.pdf) located at www.abracon.com/Support/quartz_crystals.pdf.

Getting Answers to Quartz Crystal Oscillator-Related Questions

This application note assumes that you are familiar with crystal oscillators. For more information about crystal resonator theory, oscillator operation theory, oscillator design considerations and examples of some common frequencies supported by these oscillators, visit the Texas Instruments website and read the TI Application Report located at <http://focus.ti.com/lit/an/spra054/spra054.pdf>.

Conclusion

It is possible to use the crystal oscillator circuits described in this application note with PolarPro and Eclipse II devices in any application where high precision frequency and low signal jitter are not required. Designers are strongly advised to follow correct PCB and component selection guidelines. Using these crystal components in the BOM reduces cost and saves board space.

Contact Information

Phone: (408) 990-4000 (US)
(905) 940-4149 (Canada)
+(44) 1932 57 9011 (Europe)
+(86) 21 6867 0273 (Asia – except Japan)
+(81) 45 470 5525 (Japan)

E-mail: info@quicklogic.com

Sales: www.quicklogic.com/sales

Support: www.quicklogic.com/support

Internet: www.quicklogic.com

Revision History

Revision	Date	Originator and Comments
A	November 2007	First release

Copyright and Trademark Information

Copyright © 2007 QuickLogic Corporation. All Rights Reserved.

The information contained in this document and is protected by copyright. All rights are reserved by QuickLogic Corporation. QuickLogic Corporation reserves the right to modify this document without any obligation to notify any person or entity of such revision. Copying, duplicating, selling, or otherwise distributing any part of this product without the prior written consent of an authorized representative of QuickLogic is prohibited.

QuickLogic and the QuickLogic logo, and PolarPro, are registered trademarks of QuickLogic Corporation; Eclipse, and Eclipse II are trademarks of QuickLogic Corporation.